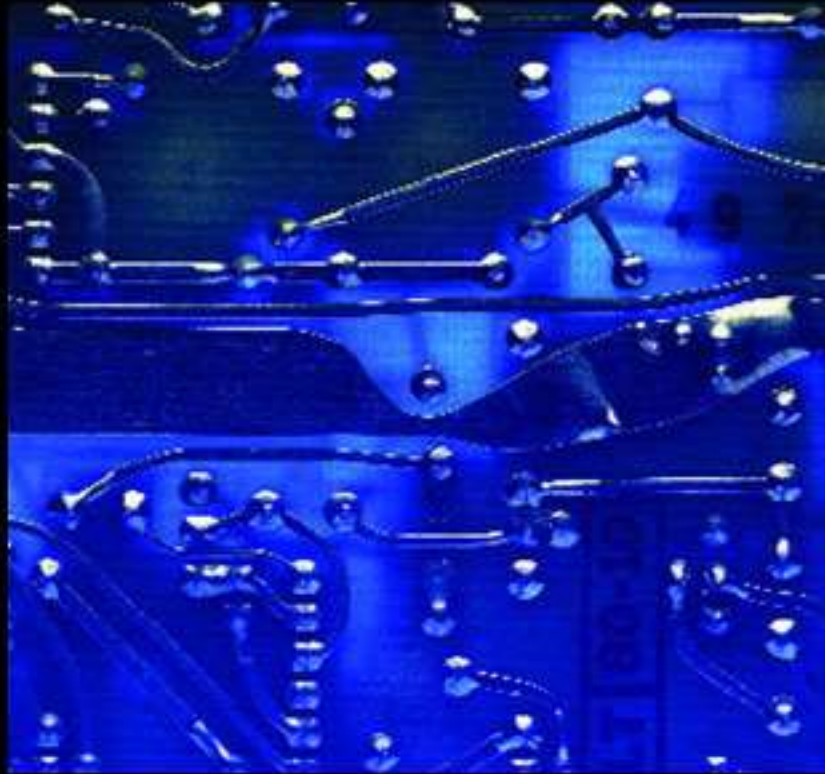


# ELECTRONIC DEVICES AND CIRCUIT THEORY

TENTH EDITION

BOYLESTAD




PEARSON

## Chapter 2: Diode Applications
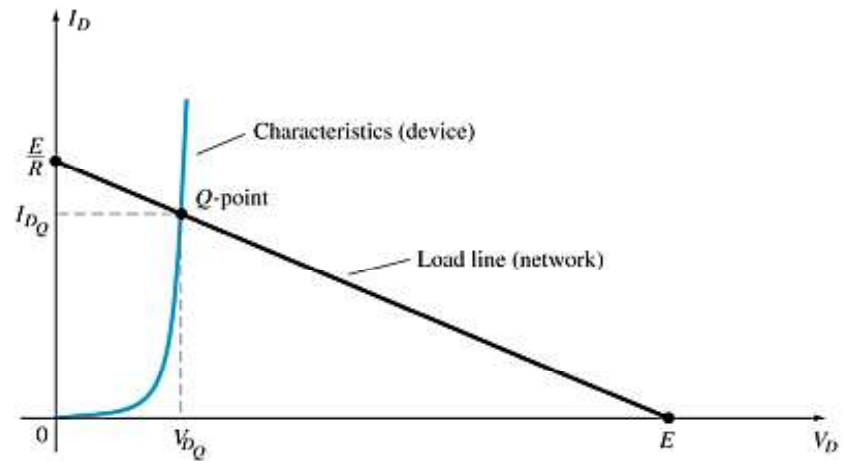
# Load-Line Analysis

The load line plots all possible combinations of diode current ( $I_D$ ) and voltage ( $V_D$ ) for a given circuit. The maximum  $I_D$  equals  $E/R$ , and the maximum  $V_D$  equals  $E$ .

The point where the load line and the characteristic curve intersect is the Q-point, which identifies  $I_D$  and  $V_D$  for a particular diode in a given circuit.



# Series Diode Configurations


## Forward Bias

### Constants

- **Silicon Diode:**  $V_D = 0.7 \text{ V}$
- **Germanium Diode:**  $V_D = 0.3 \text{ V}$
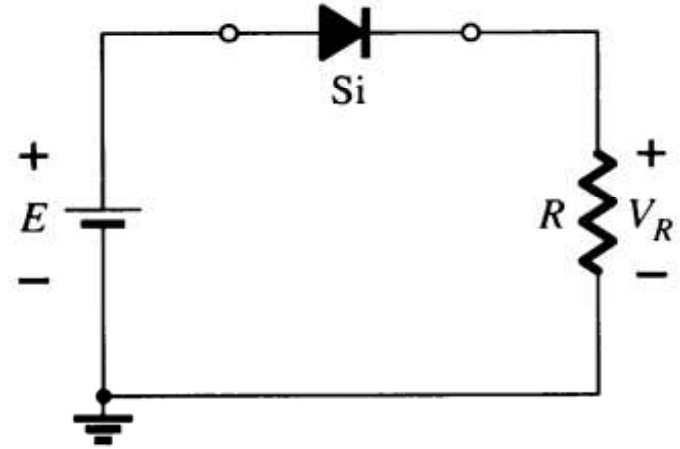
### Analysis (for silicon)

- $V_D = 0.7 \text{ V}$  (or  $V_D = E$  if  $E < 0.7 \text{ V}$ )
- $V_R = E - V_D$
- $I_D = I_R = I_T = V_R / R$




# Series Diode Configurations

## Reverse Bias

Diodes ideally behave as open circuits
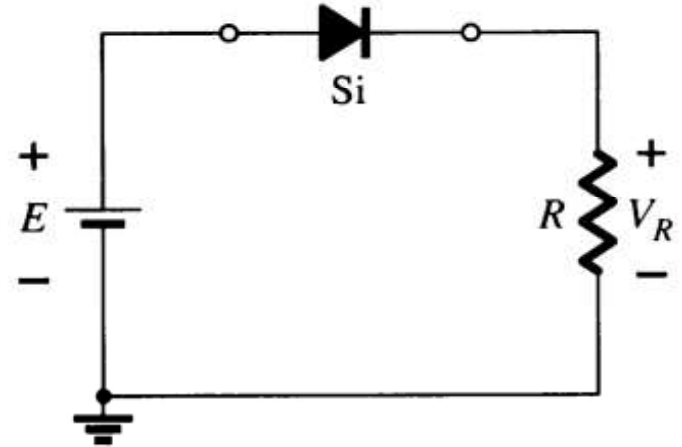
### Analysis

- $V_D = E$
- $V_R = 0 \text{ V}$
- $I_D = 0 \text{ A}$



# Parallel Configurations


$$V_D = 0.7 \text{ V}$$

$$V_{D1} = V_{D2} = V_O = 0.7 \text{ V}$$

$$V_R = 9.3 \text{ V}$$


$$I_R = \frac{E - V_D}{R} = \frac{10 \text{ V} - .7 \text{ V}}{.33 \text{ k}\Omega} = 28 \text{ mA}$$
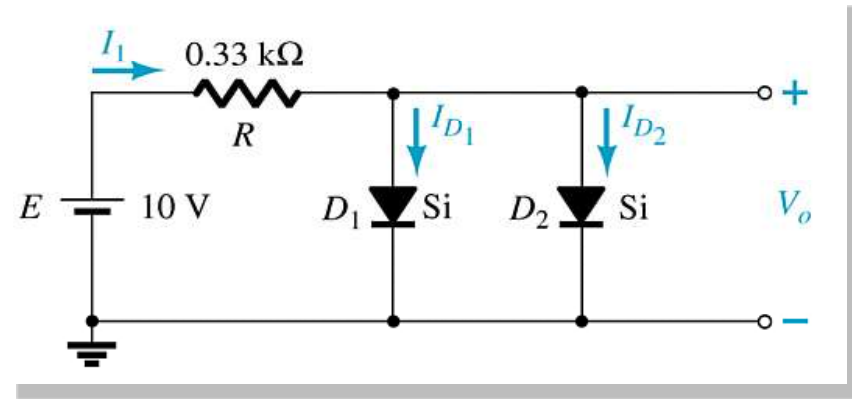
$$I_{D1} = I_{D2} = \frac{28 \text{ mA}}{2} = 14 \text{ mA}$$


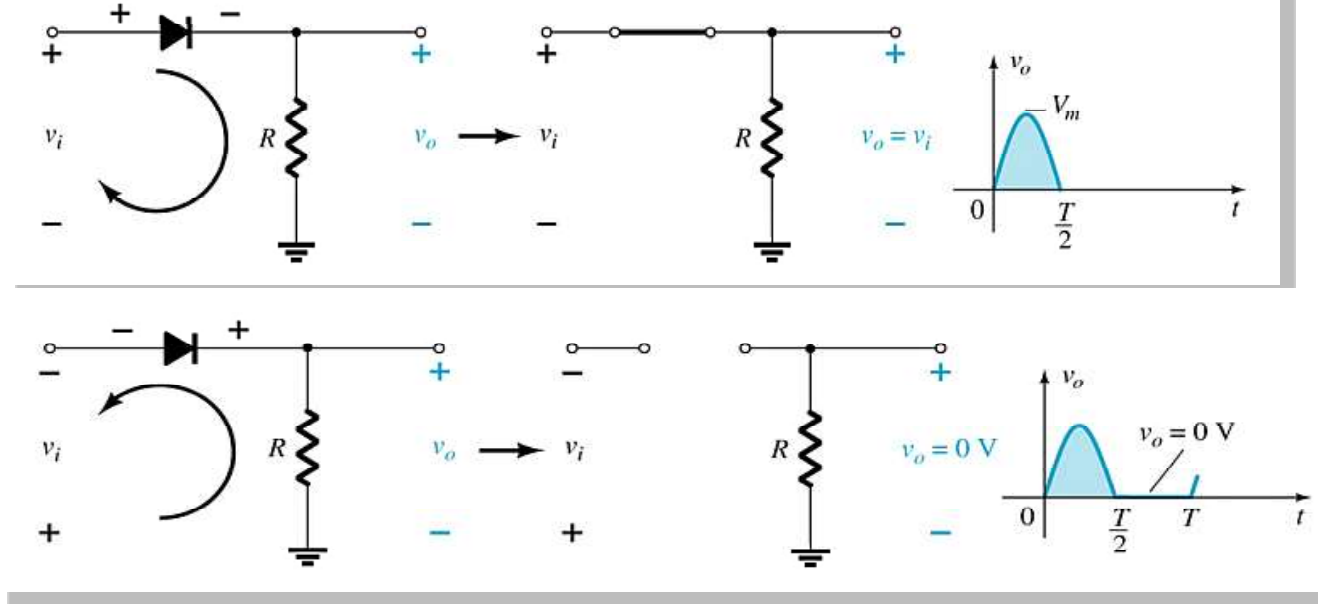
# Half-Wave Rectification

The diode only conducts when it is forward biased, therefore only half of the AC cycle passes through the diode to the output.



The DC output voltage is  $0.318V_m$ , where  $V_m$  = the peak AC voltage.

# PIV (PRV)

**Because the diode is only forward biased for one-half of the AC cycle, it is also reverse biased for one-half cycle.**

**It is important that the reverse breakdown voltage rating of the diode be high enough to withstand the peak, reverse-biasing AC voltage.**

$$\text{PIV (or PRV)} > V_m$$


- **PIV = Peak inverse voltage**
- **PRV = Peak reverse voltage**
- **$V_m$  = Peak AC voltage**

# Full-Wave Rectification

The rectification process can be improved by using a full-wave rectifier circuit.


Full-wave rectification produces a greater DC output:

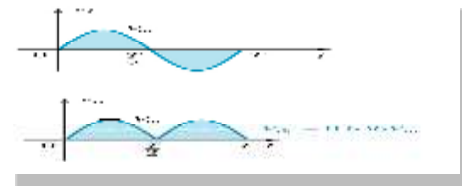- **Half-wave:**  $V_{dc} = 0.318V_m$
- **Full-wave:**  $V_{dc} = 0.636V_m$






# Full-Wave Rectification

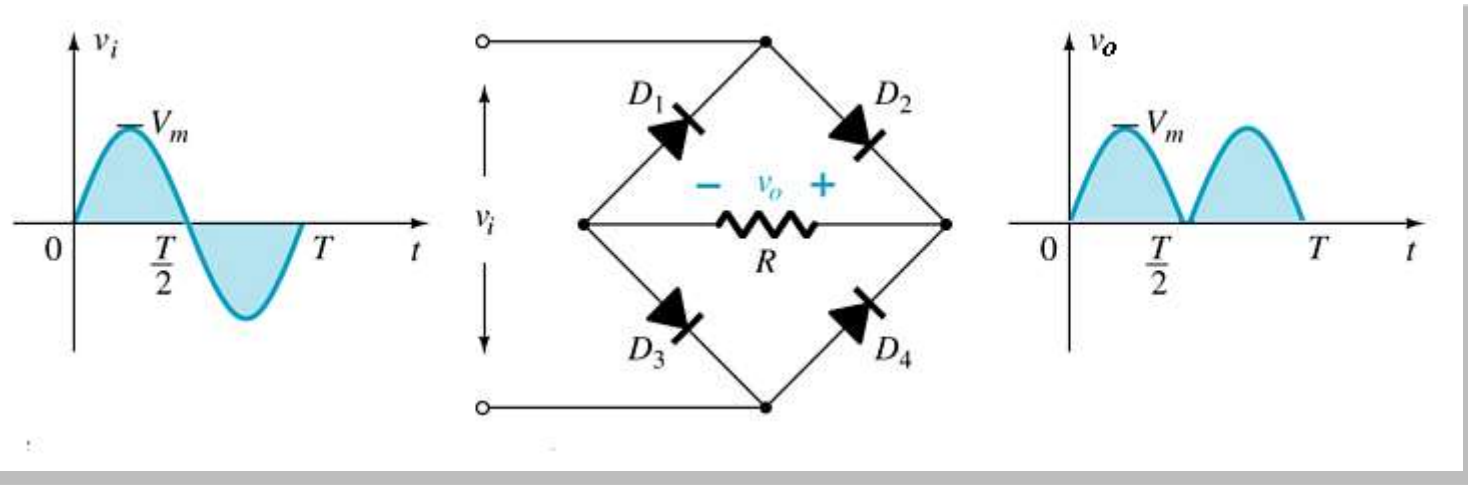

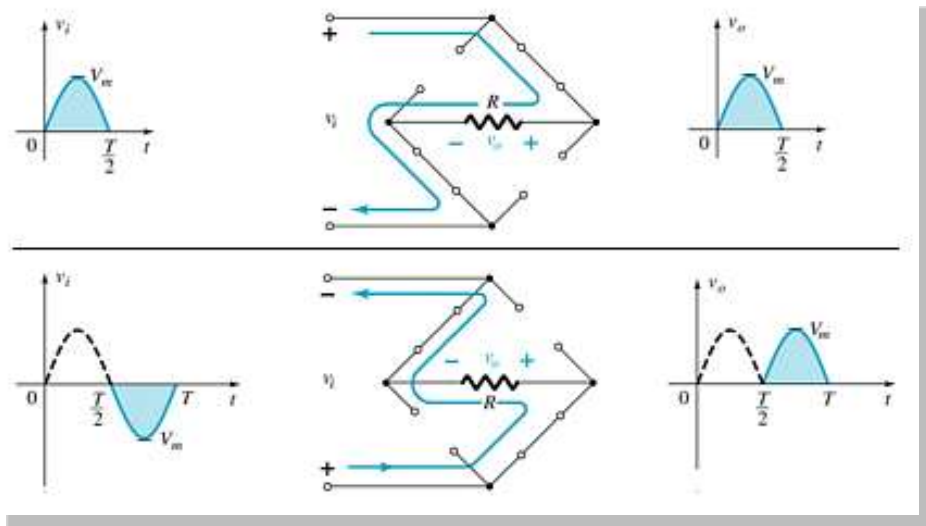
## Bridge Rectifier

- Four diodes are connected in a bridge configuration
- $V_{DC} = 0.636V_m$



# Full-Wave Rectification

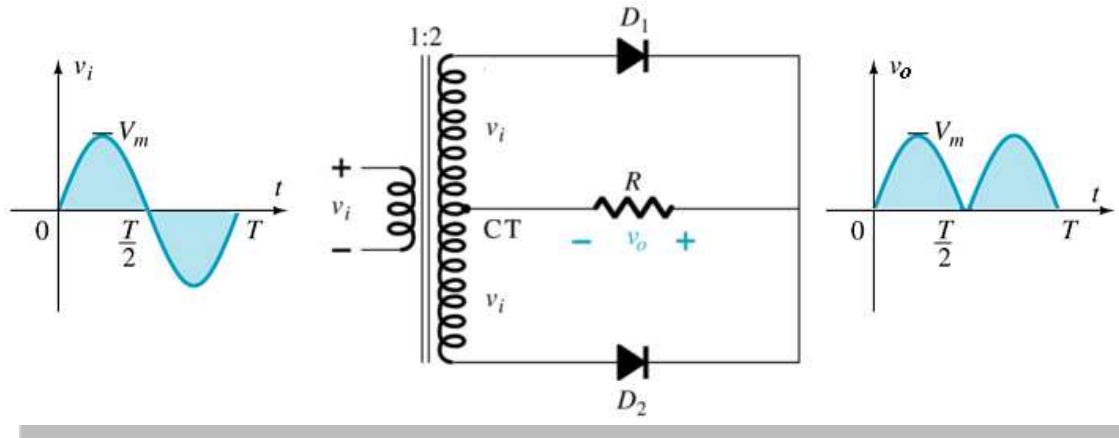


## Center-Tapped Transformer Rectifier

Requires

- Two diodes
- Center-tapped transformer

$$V_{DC} = 0.636V_m$$

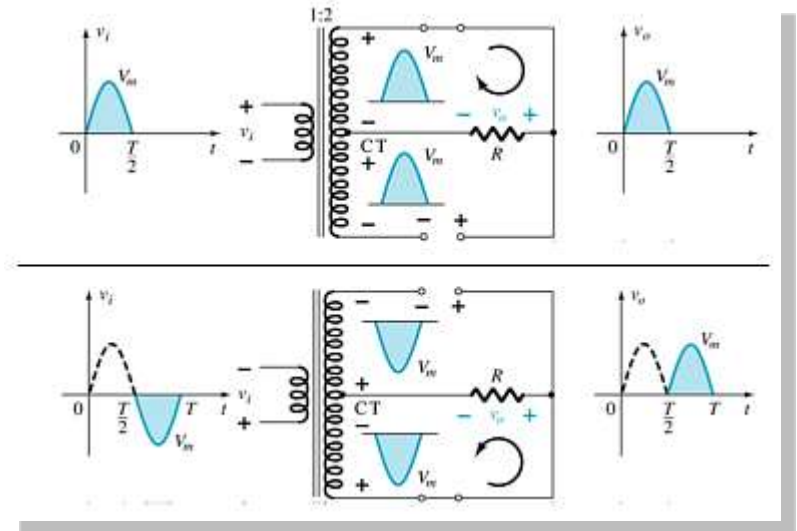

# Summary of Rectifier Circuits

Rectifier	Ideal $V_{DC}$	Realistic $V_{DC}$
Half Wave Rectifier	$V_{DC} = 0.318V_m$	$V_{DC} = 0.318V_m - 0.7$
Bridge Rectifier	$V_{DC} = 0.636V_m$	$V_{DC} = 0.636V_m - 2(0.7 \text{ V})$
Center-Tapped Transformer Rectifier	$V_{DC} = 0.636V_m$	$V_{DC} = 0.636V_m - 0.7 \text{ V}$


$V_m$  = peak of the AC voltage.

In the center tapped transformer rectifier circuit, the peak AC voltage is the transformer secondary voltage to the tap.
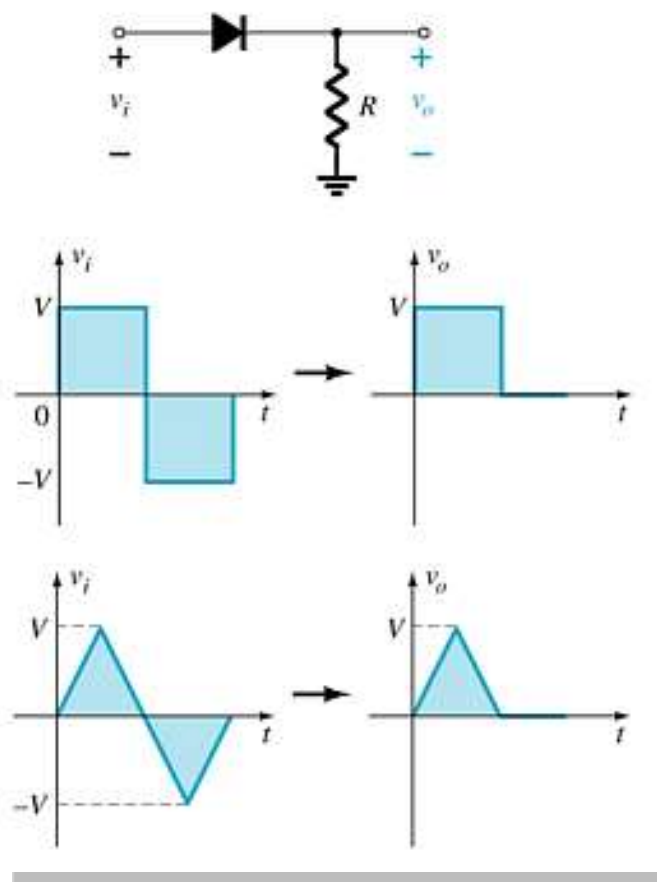
# Diode Clippers




The diode in a **series clipper** “clips” any voltage that does not forward bias it:

- A reverse-biasing polarity
- A forward-biasing polarity less than 0.7 V (for a silicon diode)


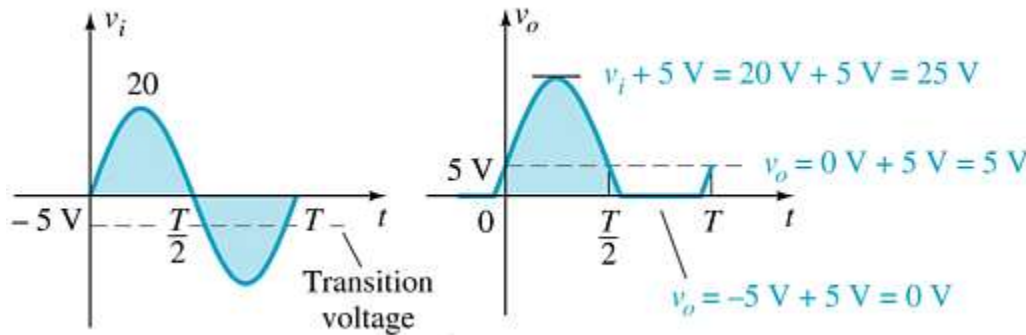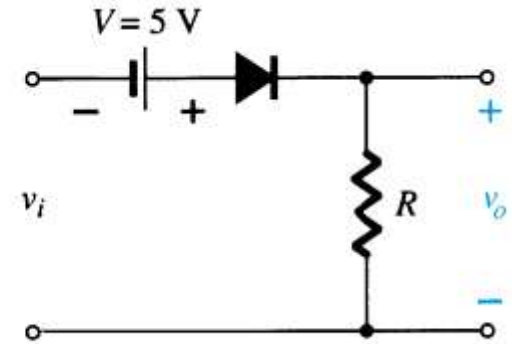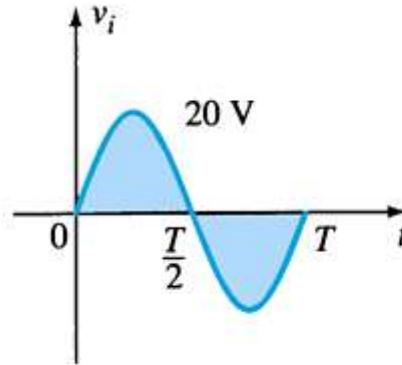
# Biased Clippers


Adding a DC source in series with the clipping diode changes the effective forward bias of the diode.


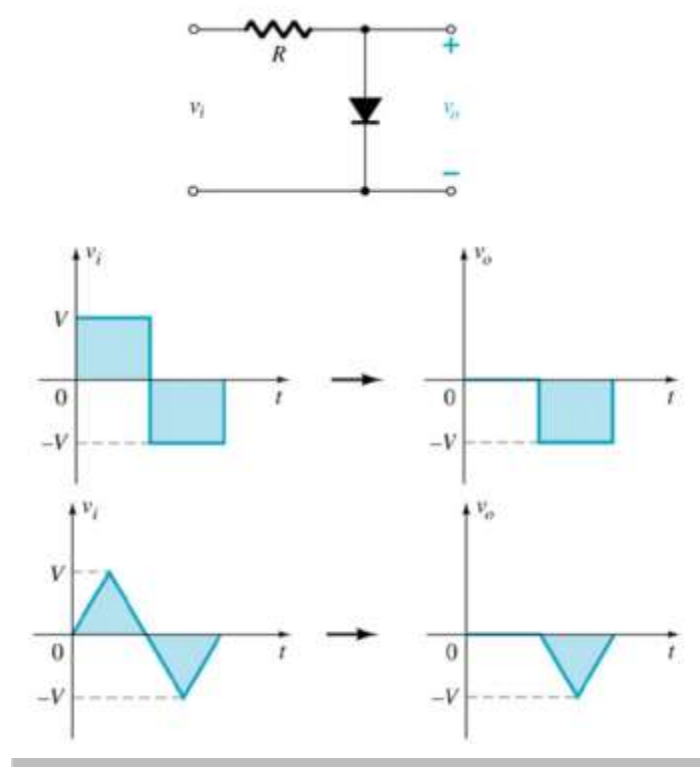
# Parallel Clippers



The diode in a **parallel clipper** circuit “clips” any voltage that forward bias it.

DC biasing can be added in series with the diode to change the clipping level.








# Summary of Clipper Circuits

Simple Parallel Clippers (Ideal Diodes)

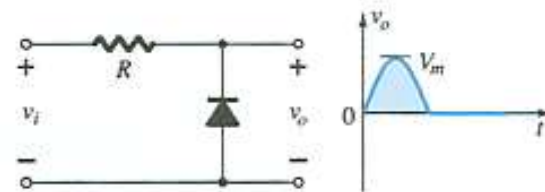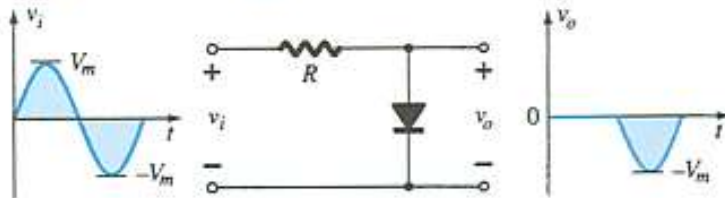

Biased Parallel Clippers (Ideal Diodes)

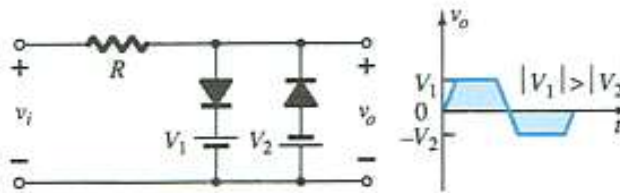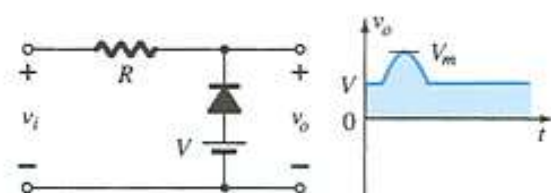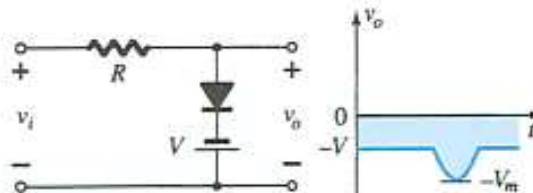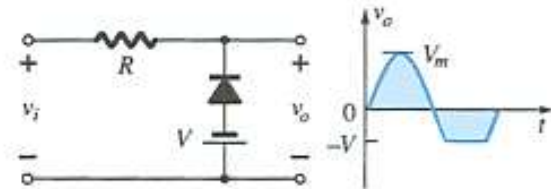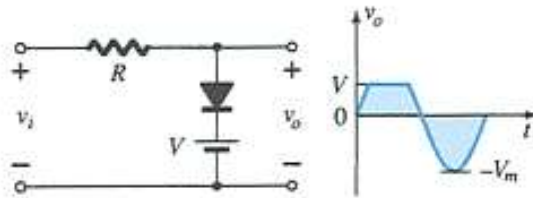


more...


# Summary of Clipper Circuits

## Simple Series Clippers (Ideal Diodes)



POSITIVE

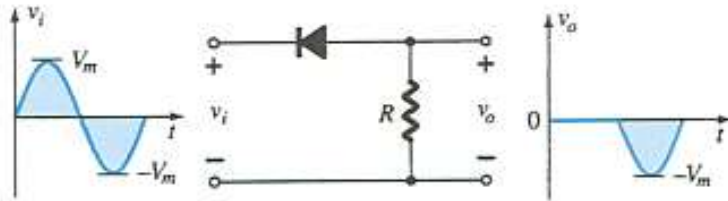

NEGATIVE

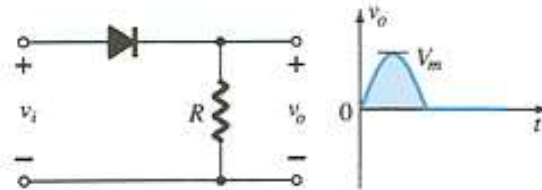


## Biased Series Clippers (Ideal Diodes)

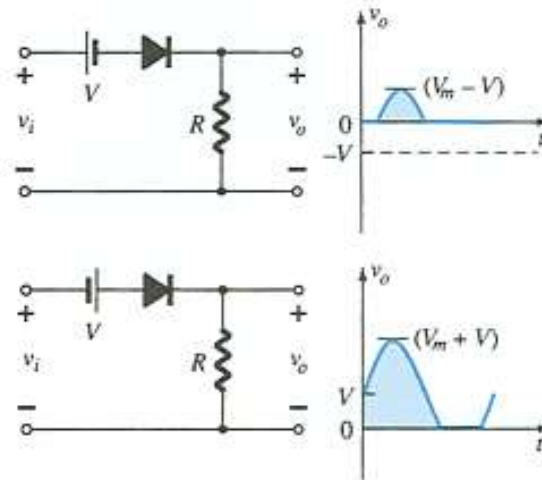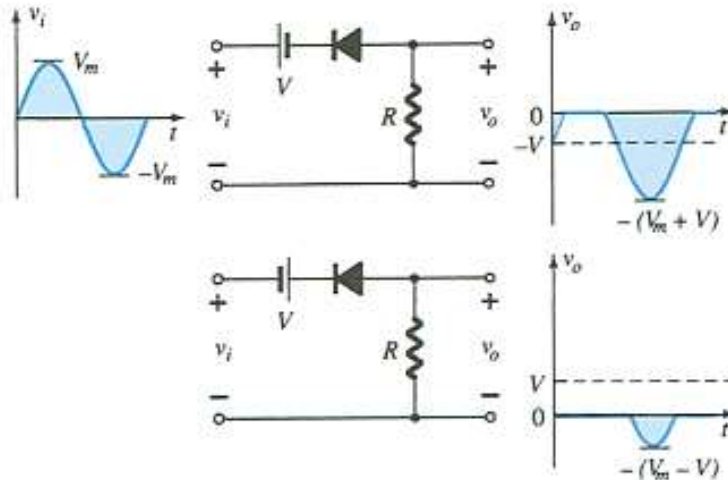


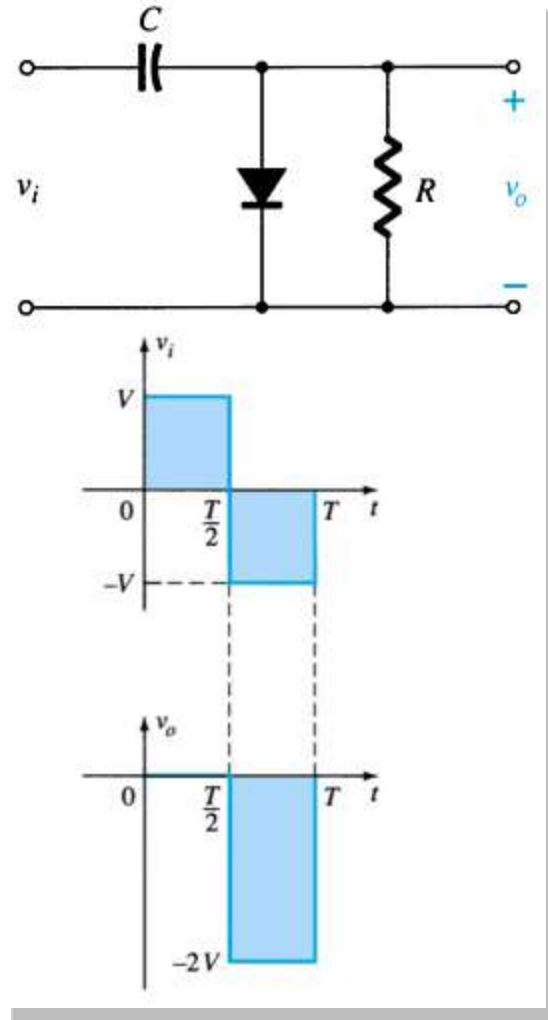
# Clampers


A diode and capacitor can be combined to “clamp” an AC signal to a specific DC level.


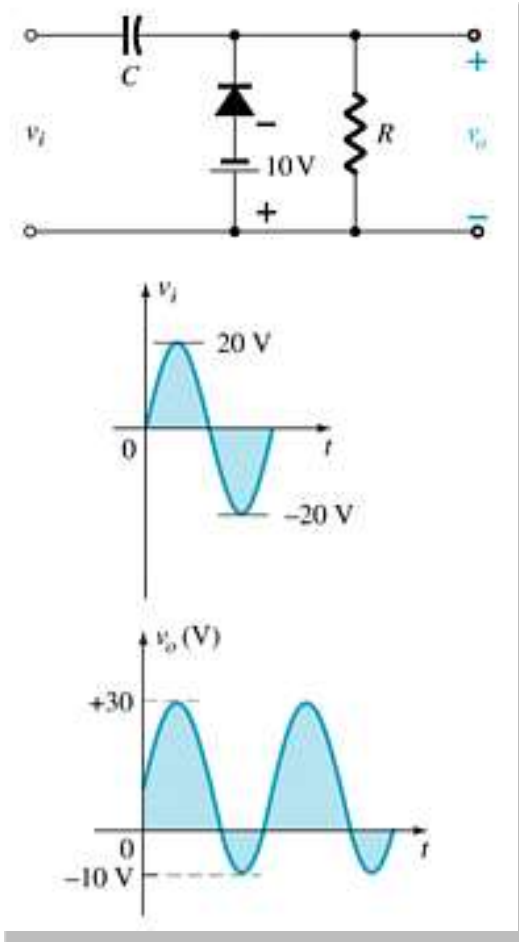
# Biased Clamper Circuits


The input signal can be any type of waveform such as sine, square, and triangle waves.

The DC source lets you adjust the DC clamping level.



# Summary of Clamper Circuits



## Clamping Networks

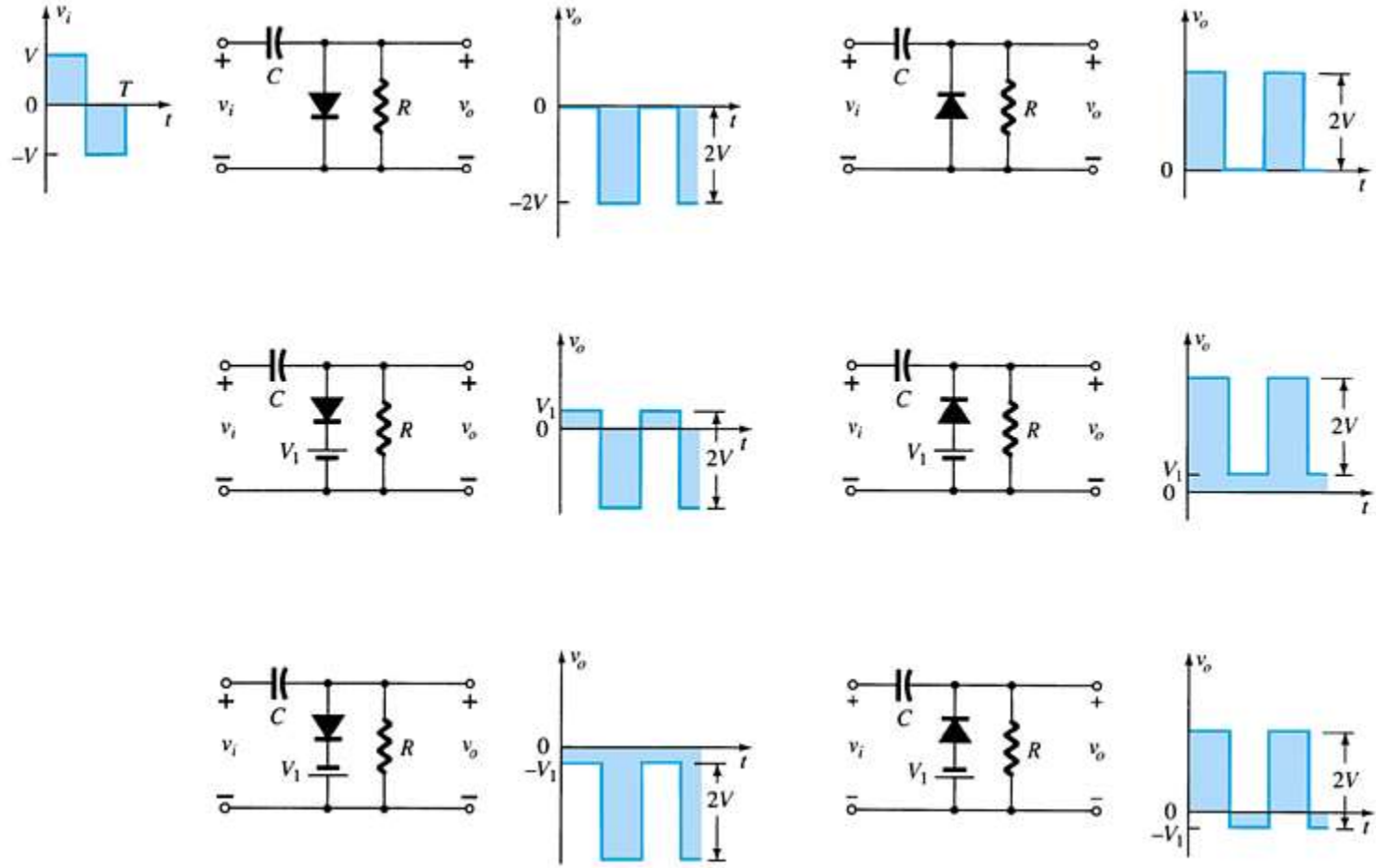
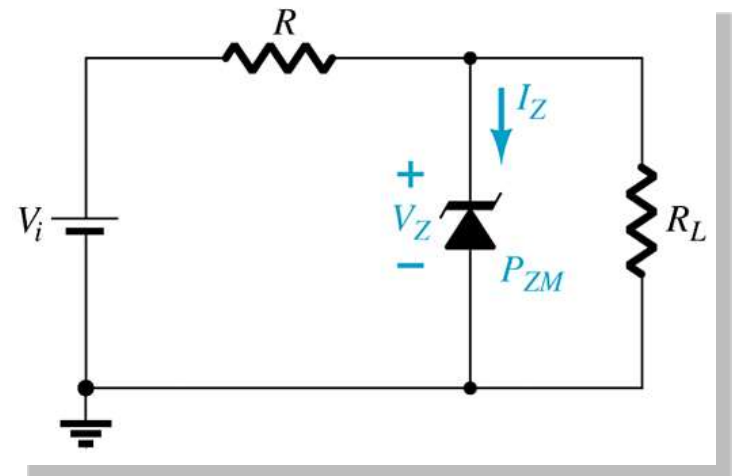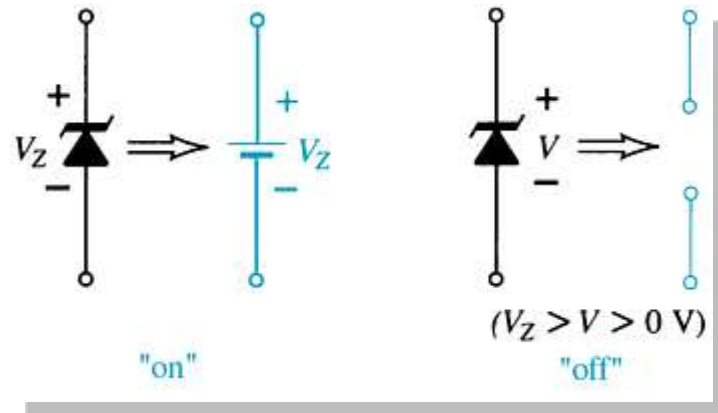
# Zener Diodes

The Zener is a diode operated in reverse bias at the Zener Voltage ( $V_Z$ ).

- When  $V_i \geq V_Z$ 
  - The Zener is on
  - Voltage across the Zener is  $V_Z$
  - Zener current:  $I_Z = I_R - I_{RL}$
  - The Zener Power:  $P_Z = V_Z I_Z$
- When  $V_i < V_Z$ 
  - The Zener is off
  - The Zener acts as an open circuit




# Zener Resistor Values

If  $R$  is too large, the Zener diode cannot conduct because the available amount of current is less than the minimum current rating,  $I_{ZK}$ . The minimum current is given by:

$$I_{L\min} = I_R - I_{ZK}$$

The *maximum* value of resistance is:

$$R_{L\max} = \frac{V_Z}{I_{L\min}}$$

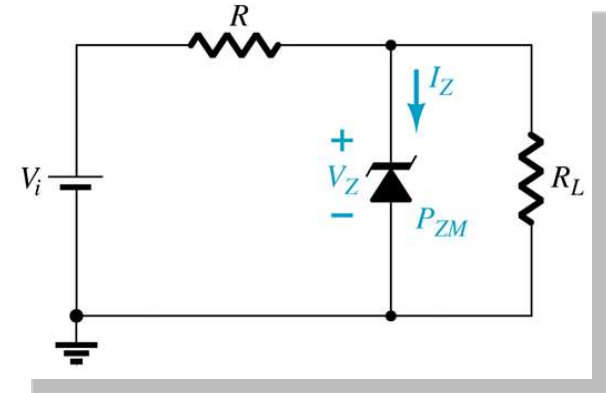

If  $R$  is too small, the Zener current exceeds the maximum current rating,  $I_{ZM}$ . The maximum current for the circuit is given by:

$$I_{L\max} = \frac{V_L}{R_L} = \frac{V_Z}{R_{L\min}}$$

The *minimum* value of resistance is:


$$R_{L\min} = \frac{RV_Z}{V_i - V_Z}$$

# Voltage-Multiplier Circuits

**Voltage multiplier circuits use a combination of diodes and capacitors to step up the output voltage of rectifier circuits.**

- **Voltage Doubler**
- **Voltage Tripler**
- **Voltage Quadrupler**

# Voltage Doubler

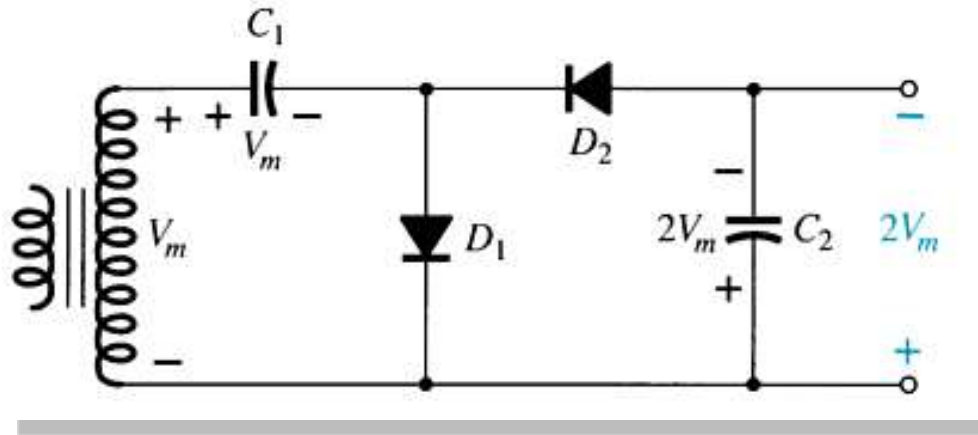

**This half-wave voltage doubler's output can be calculated by:**


$$V_{\text{out}} = V_{C2} = 2V_m$$

**where  $V_m$  = peak secondary voltage of the transformer**

# Voltage Doubler


- **Positive Half-Cycle**
  - $D_1$  conducts
  - $D_2$  is switched off
  - Capacitor  $C_1$  charges to  $V_m$
- **Negative Half-Cycle**
  - $D_1$  is switched off
  - $D_2$  conducts
  - Capacitor  $C_2$  charges to  $V_m$

$$V_{\text{out}} = V_{C2} = 2V_m$$

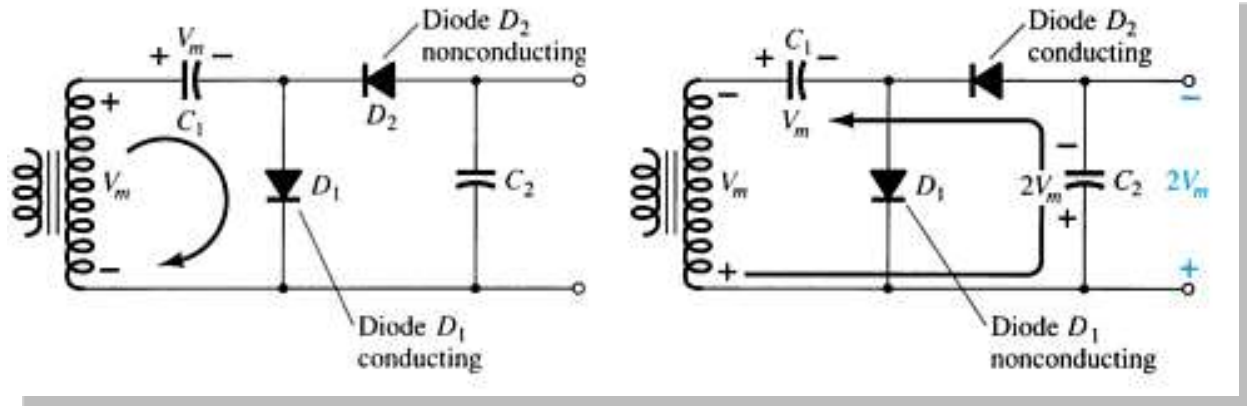



# Voltage Tripler and Quadrupler

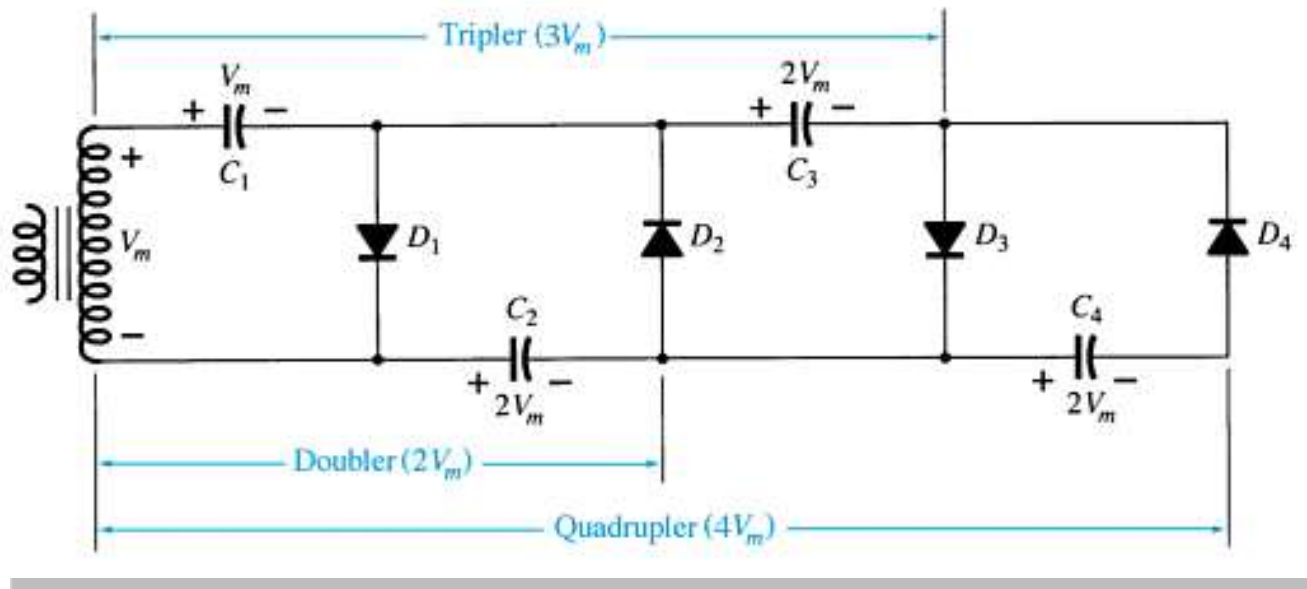

# Practical Applications

- **Rectifier Circuits**
  - **Conversions of AC to DC for DC operated circuits**
  - **Battery Charging Circuits**
- **Simple Diode Circuits**
  - **Protective Circuits against**
  - **Overcurrent**
  - **Polarity Reversal**
  - **Currents caused by an inductive kick in a relay circuit**
- **Zener Circuits**
  - **Overvoltage Protection**
  - **Setting Reference Voltages**